



LUND  
UNIVERSITY

EITP25 2020


# Lecture 2 – Current Memory Technologies

---



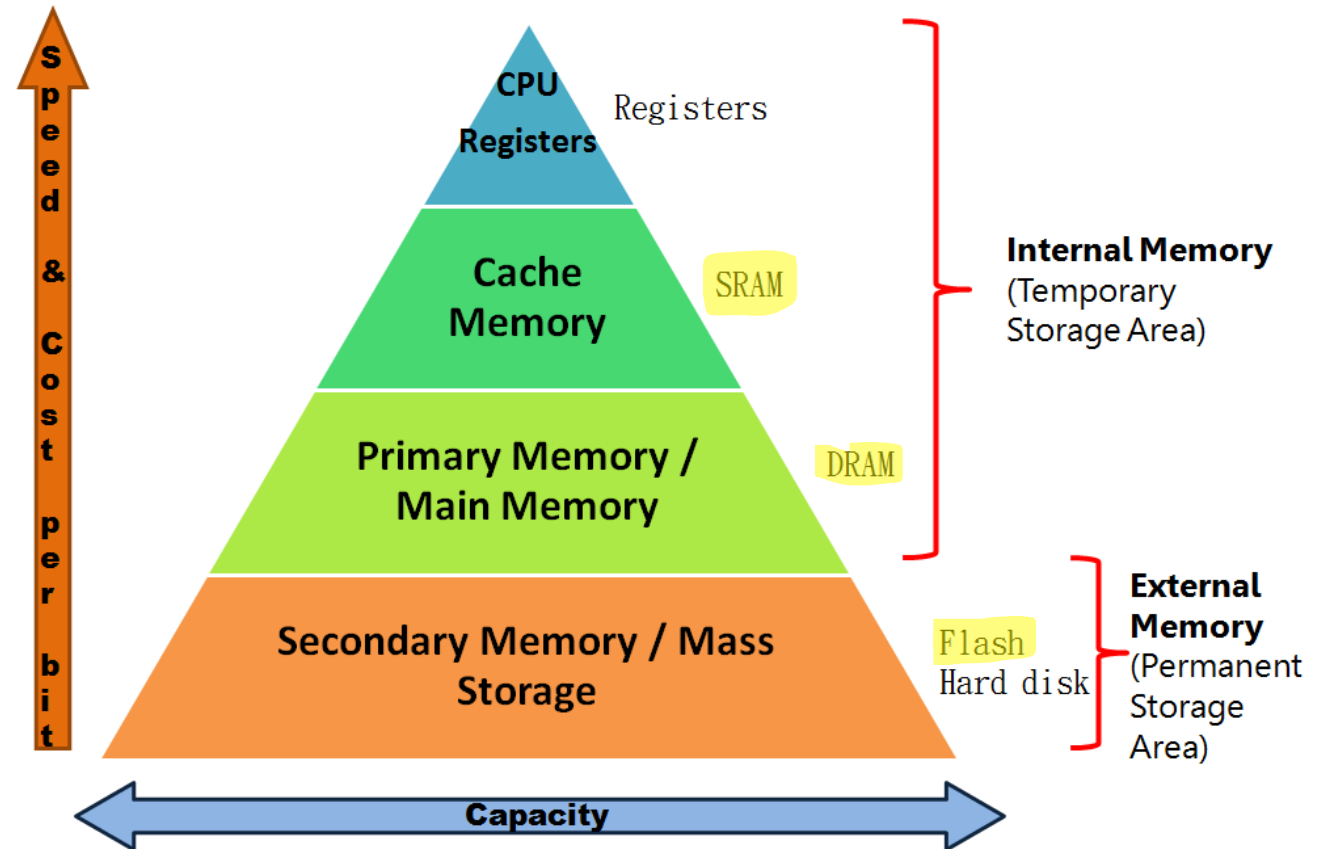
# Outline


- Physics of charge-based memory
- DRAM
- Flash memory
- SRAM



# Charge-based storage

 
 
# 2 min exercise – QD as 10 year storage?



$$m_e = 0.08m_0$$

$$E_b = 0.75 \text{ eV}$$


$$L^2 = 100 \text{ nm}^2$$

$$kT = 1/40 \text{ eV}$$

What is the emission retention time?

$$\text{Emission: } t_r = \frac{1}{L^2 f_0} \exp\left(\frac{E_b}{kT}\right)$$


 
$$(\text{Tunneling: } t_T = \frac{1}{L^2 f_0^*} \exp\left(\frac{2\sqrt{2m_e E_b}}{\hbar} a\right))$$



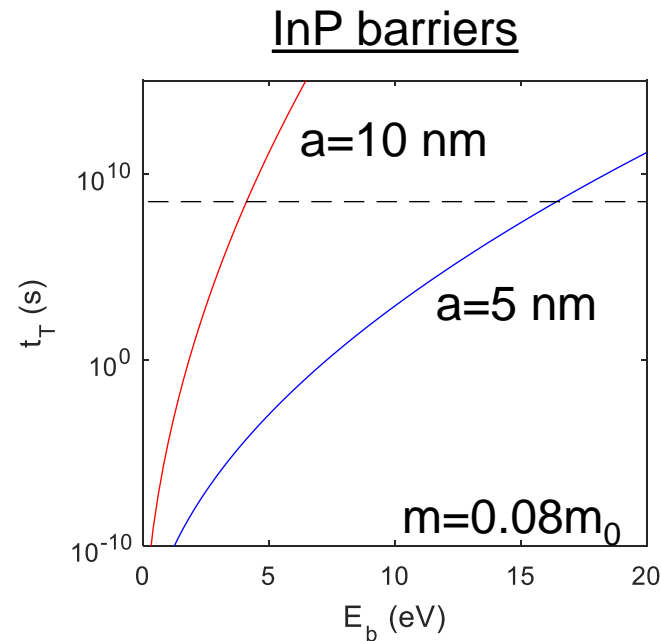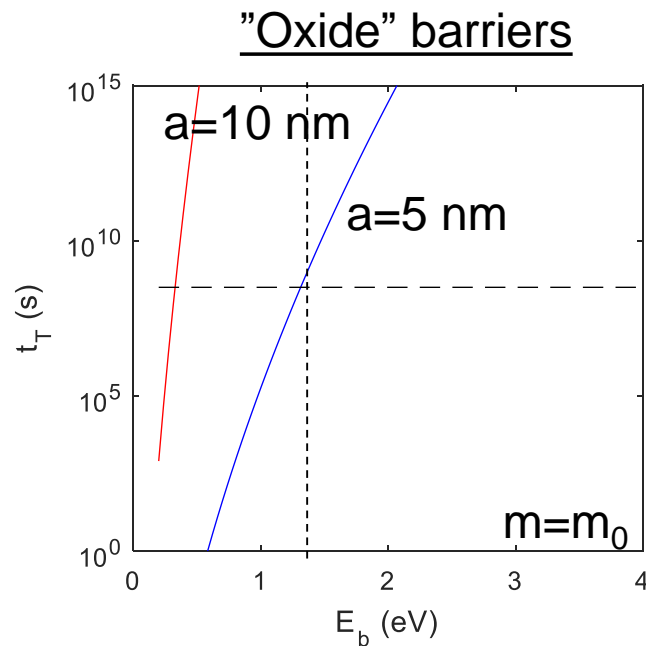
# What kind of barrier is needed?

- For emission  $E_b > 1.4$  eV for  $t_r > 10$  years.
- Assuming  $t_{\text{I}} < t_r \rightarrow a > 5$  nm for oxide barrier

$$t_T = \frac{1}{L^2 f_0^*} \exp\left(\frac{2\sqrt{2m_e E_b}}{\hbar} a\right) \quad L = 10 \text{ nm}$$





 → Hard to achieve 10 year retention with semiconductor barriers...but ms?



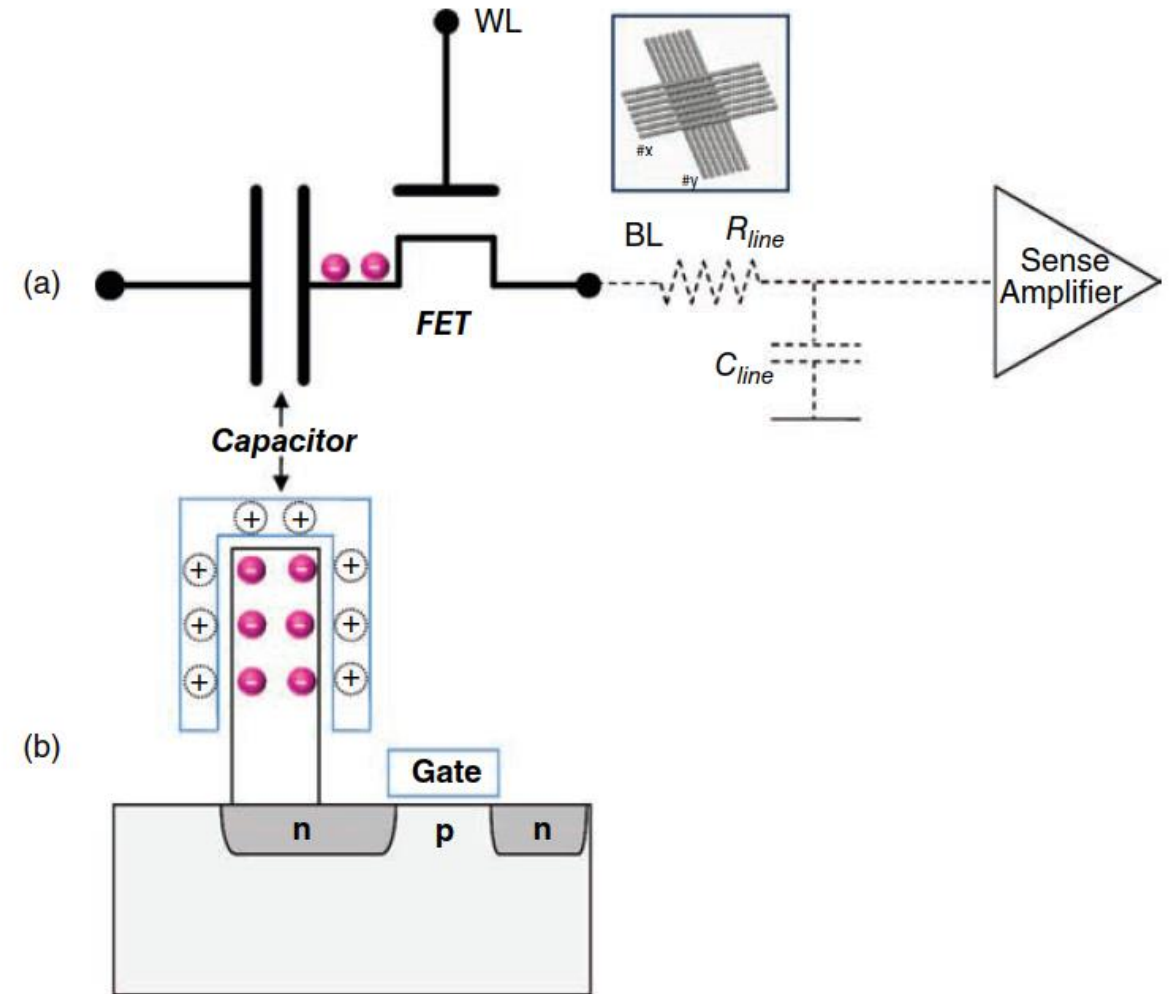 
# Dynamic Random Access Memory

- 1 transistor + 1 capacitor (1T1C)
- Charge stored on capacitor  $\rightarrow$  memory bit
- Retention time limited by Si band gap (1.1 eV)  
~ milliseconds




# DRAM write a "1"

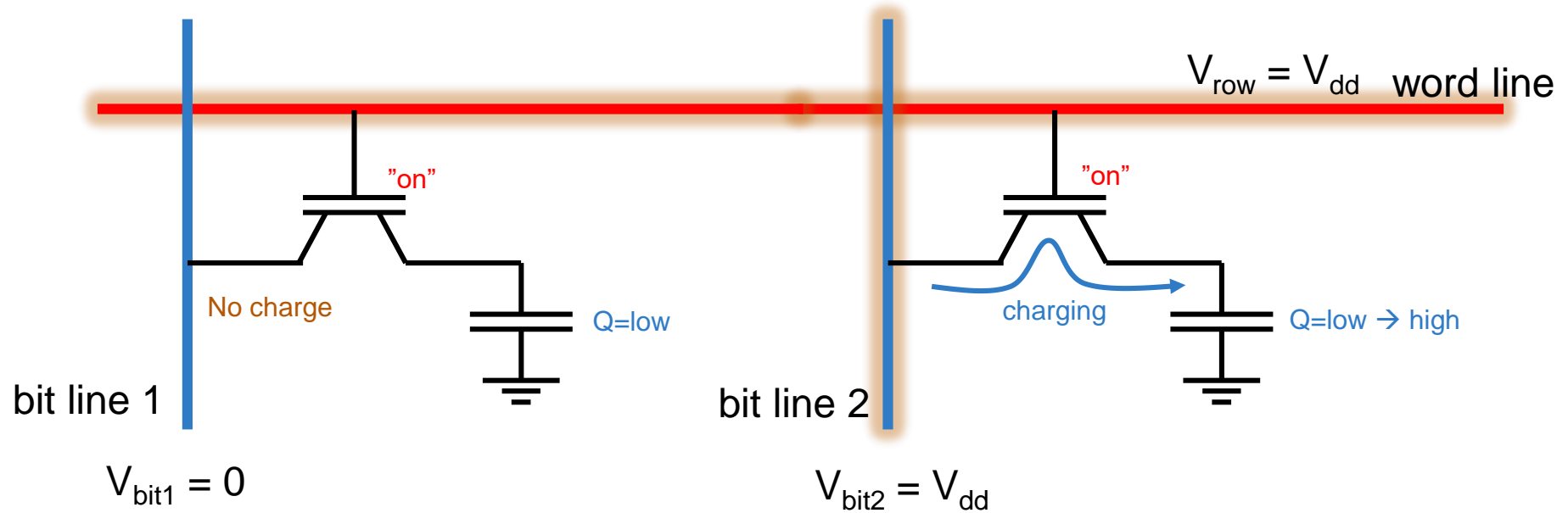

1. Drive bit line to  $V_{dd}$
2. Select word line
3. Capacitor is charged and the state is saved.


# DRAM read a bit – step 1

 

1. Precharge bit line to  $V_{\text{dd}}/2$ 
  - Reduces read swing








# DRAM read a bit – step 2

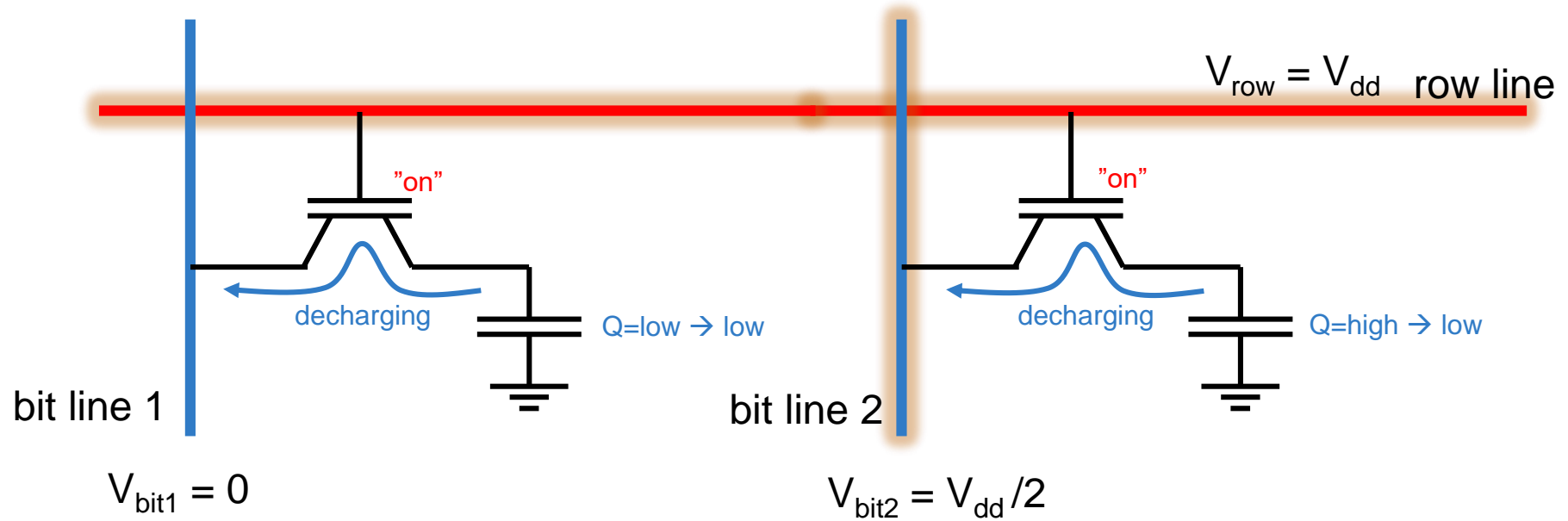

1. Precharge bit line to  $V_{\text{dd}}/2$
2. Select the word line
  - Capacitors on whole row discharge (destructive read)
3. Finish by re-writing data on row

# Water pond model

     
- (1) Fill the ditch and open the tap to fill pond.
- (2) Close the tap to store the water.
- (3) Water is lost by evaporation and must be refilled.
- (4) Opening tap to measure if there is water empties pond


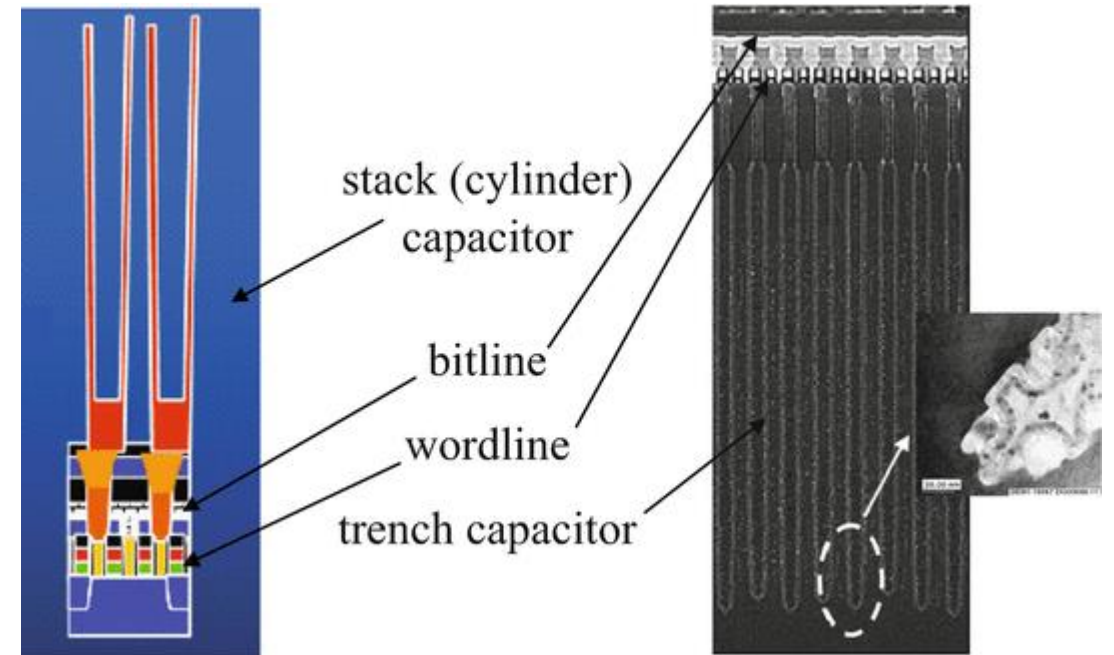
# DRAM implementation

- Two main types of capacitor implementations:
  - 1) Stacked (above FET)
    - May interfere with metal routing
    - Done after logic
    - Two cells can share same BL  $\rightarrow$   $6F^2$  possible
  - 2) Trench (below FET)
    - Done prior to logic (must survive high T)
    - Hard to control depth by dry etching
    - No interference with interconnects
    - Not as scalable ( $8F^2$ )

Requires at least 25 fF capacitance for read-out  
 $\rightarrow$  How high capacitors are needed?



# Example – Capacitor height

**Table 3.1** Resistances and capacitances in DRAM


$F$ (nm)	90	70	60	50	40	20	10
$R_C$ ( $\Omega$ ) <sup>a</sup>	210	527	928	1840	4380	$1.15 \times 10^5$	$1.37 \times 10^8$
$R_{\text{FET}}$ ( $\Omega$ ) <sup>b</sup>	2770	3560	4150	4980	6220	12 400	22 600
$R_{\text{line}}$ ( $\Omega$ ) <sup>c</sup>	144	192	228	284	374	932	2600
$C_{\text{line}}$ (fF) <sup>d</sup>	55	50	45	40	35	24	16
$C_{\text{cell}}$ (fF)	25	25	25	25	25	25	25

<sup>a</sup> Serial resistance of an idealized cell capacitor [3].

<sup>b</sup> Channel resistance of an idealized FET in ON state [3].

<sup>c</sup> Line resistance in  $256 \times 256$  array (see Appendix).
 
<sup>d</sup> Line capacitance in  $256 \times 256$  array (see Appendix).



# Energy usage of DRAM


- Write energy:

- $E_{DRAM} = (C_{line} + C_{cell})V_{cell}^2 + C_{line}V_g^2$

"pump"  $N \sim 10^5$  (25 fF)  
electrons through BL ( $C_{line}$ )  
to charge capacitor ( $C_{cell}$ )

Energy for  
controlling the gate  
of FET via WL

 
- Additional cost for refreshing memory (retention)
  - Average access interval  $t_a \sim 1 - 10s$
  - Retention time,  $t_r \sim 50 - 100 ms$
- $E_{TOT} = E_{DRAM} + \frac{t_a}{t_r} E_{DRAM} = \left(1 + \frac{t_a}{t_r}\right) E_{DRAM} \sim \underline{30-60 pJ}$



# DRAM access time

$$t_{DRAM} = (R_{cap} + R_{FET,on} + R_{line})(C_{cap} + C_{line})$$

Space-Action metric: energy x volume x access

 

**Table 3.2** Scaling and performance projections for DRAM

Parameter		Current node	Minimal node	Optimal <sup>a</sup> node
Feature size <i>F</i>		28–45 nm	>10 nm <sup>b</sup>	45 nm
Access time	Practical	<10 ns	>25 ns	<10 ns
	RC limit	0.5–2 ns	25 ns <sup>c</sup>	0.5 ns
Retention time		64 ms	64 ms	64 ms
Write cycles		>10 <sup>16</sup>	>10 <sup>16</sup>	>10 <sup>16</sup>
Operating voltage		~2 V	~2 V	~2 V
Number of stored electrons		10 <sup>5</sup>	10 <sup>5</sup>	10 <sup>5</sup>
Write energy (J bit <sup>-1</sup> )	Cell level	10 <sup>-14</sup>	10 <sup>-14</sup>	10 <sup>-14</sup>
	Array level	10 <sup>-13</sup>	10 <sup>-13</sup>	10 <sup>-13</sup>
	System level	(3–6) × 10 <sup>-11</sup>	>10 <sup>-11</sup>	(3–6) × 10 <sup>-11</sup>

<sup>a</sup> Corresponds to the minimum of the Energy–Space–Time product.  
<sup>b</sup> Limited by the dimensions of the cell capacitor; “minimal” only refers to the node size and area (in this case, the timing and energy for “minimal” is greater than “current” or “optimal” nodes).  
<sup>c</sup> Expected RC delay at 16 nm.

→ DRAM has a scaling limit due to growing series resistance of capacitor.

# Flash memory



1 – 4 TB

SSD harddrives






USB sticks



phones

  
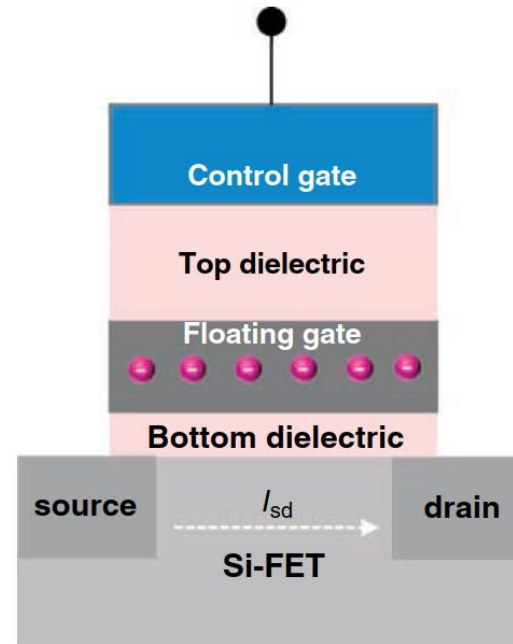
# Flash memory cell

- Charges trapped in a floating gate  
→ memory state
- Read out by  $V_T$  shift in n-MOSFET
- Barriers by dielectrics  
→  $E_b \sim 3 \text{ eV}$  → non-volatile
- Read/write performed by "bending" barriers by biasing






# Different types of Flash

 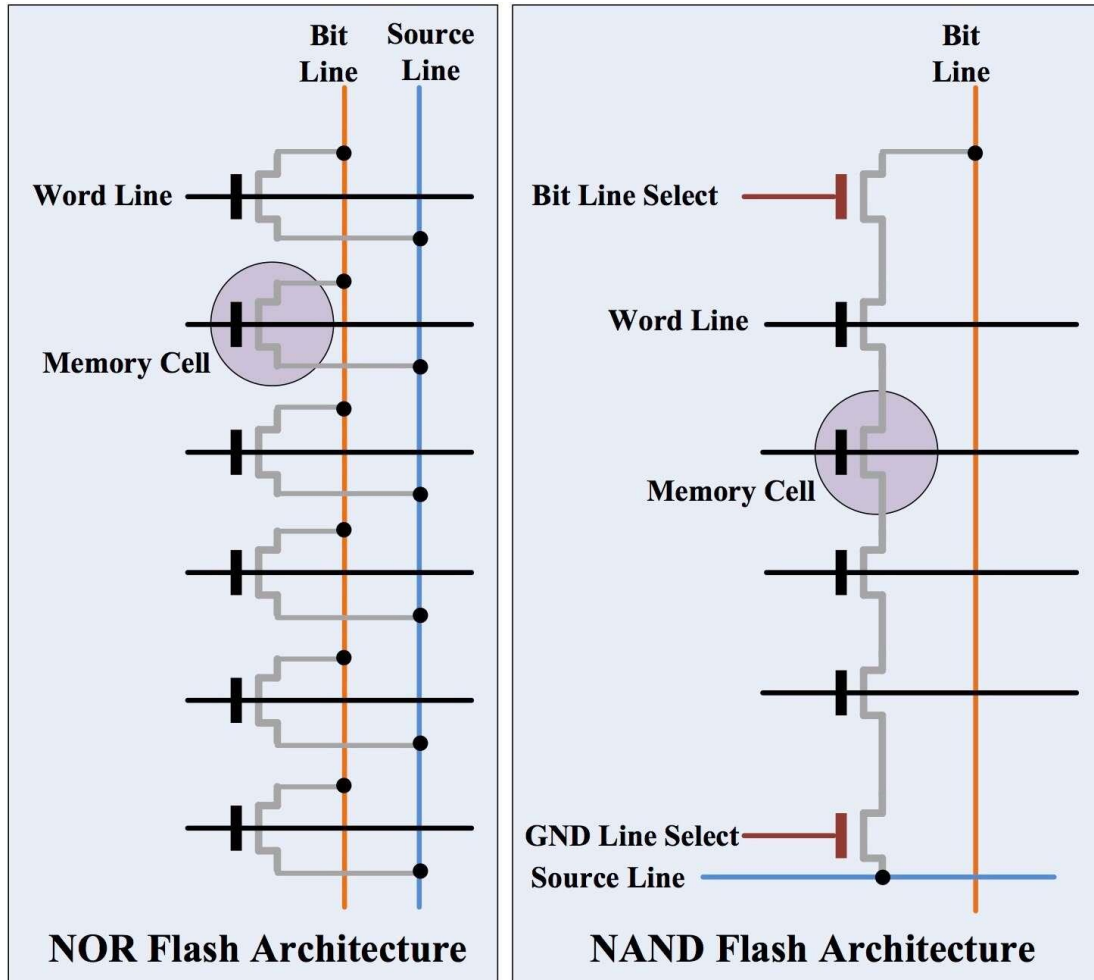


**3D NAND Flash**

# Flash operation

 

 
## Write by direct tunneling

- $V_{\text{write}} > 2E_b/q \sim \mathbf{6-15\ V}$
- Barrier  $\rightarrow$  triangular
- Tunneling into island
- Used by NAND


 
## Read




- $V_{\text{read}} < 2E_b/q \sim \mathbf{4-5\ V}$
- FET current senses charge state
- $V_T$  shifted by charge



## Write by hot electron injection

- High  $V_{\text{DS}} > E_b/q \sim 3-4\ \text{V}$
- Injection above barrier
- Limits shortest L. **Why?**
- Faster than tunneling
- Used by NOR

# Reading Flash

   

# Energy usage Flash

## WRITE by Direct tunneling

- **Bend barriers + pump charge onto island:**
- $E_{DT} = \frac{C_1 C_2}{C_1 + C_2} V_{write}^2 + q N_{el} V_{write}$

## WRITE by Hot electron injection

- **Inefficient:  $1e^-$  per  $10^5$ - $10^6$  are injected ( $\eta = I_{GS}/I_{DS}$ )**
- $E_{HEI} = \frac{1}{\eta} N_{el} * q V_{ds}$

Large  $V_{write} \rightarrow$  System energy consumption limited by line charging and peripheral circuitry

# Summary Flash

**Table 3.4** Scaling and performance projections for Flash memory

Parameter		NAND		NOR	
		Current	Minimal	Current	Minimal
Feature size $F$		16–32 nm	>10 nm	45 nm	25 nm
Access time	Write <sup>a</sup>	~100 $\mu$ s	~100 $\mu$ s	~10 $\mu$ s <sup>c</sup>	~10 $\mu$ s
	Read <sup>b</sup>	~10 $\mu$ s <sup>c</sup>	~10 $\mu$ s	60–120 ns <sup>c</sup>	~60 ns
Retention time		10 yr	<10 yr	10 yr	10 yr
Write cycles		~10 <sup>5</sup>	<10 <sup>4</sup>	~10 <sup>5</sup>	~10 <sup>5</sup>
Operating voltage	Write	15–20	15	8–10	~8
	Read	5	5	5	5
Number of stored electrons		~50	~10	~200	~100
Write energy (J bit <sup>-1</sup> )	Cell level	$4 \times 10^{-16}$	~10 <sup>-16</sup>	$2 \times 10^{-10}$	~10 <sup>-10</sup>
	Array level	$10^{-11}$ – $10^{-12}$	~10 <sup>-12</sup>	$>2 \times 10^{-10}$	$>10^{-10}$
	System level	$10^{-10}$ – $10^{-9}$ <sup>d</sup>	10 <sup>-10</sup> –10 <sup>-9</sup>	~10 <sup>-9</sup> <sup>e</sup>	~10 <sup>-9</sup>

NOR scales worse  
10F<sup>2</sup> vs 4F<sup>2</sup>



NOR is much faster

NAND cell write is  
more efficient


But on system level  
they are equal
  
# Static Random Access Memory


- Fastest memory there is
- Used for registers, caches
- Takes up ~ half of chip area
- Principle: 2 CMOS inverters connected back to back
- Transistor performance matching is crucial!
- 6 transistors per cell ~  $140F^2$



# SRAM as charge based memory

 


# SRAM write

 

1. Apply "bit" to bit line BL: "1"
  - And opposite to conjugate BL




# SRAM write

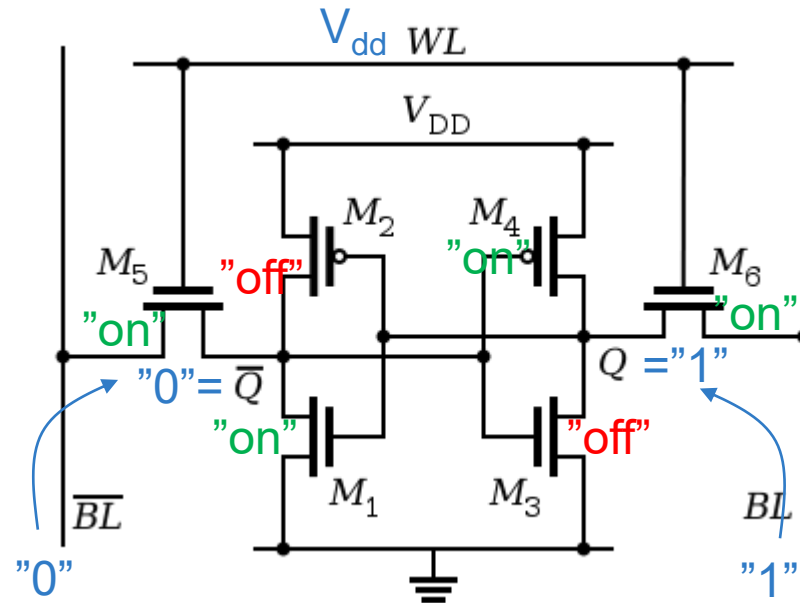


1. Apply "bit" to bit line BL: "1"
2. Turn on M5 and M6 **via WL** to save bit
  - M5 saves on right inverter
  - M6 saves on left inverter
  - M5/6 are stronger (larger) than M1-4

# SRAM read

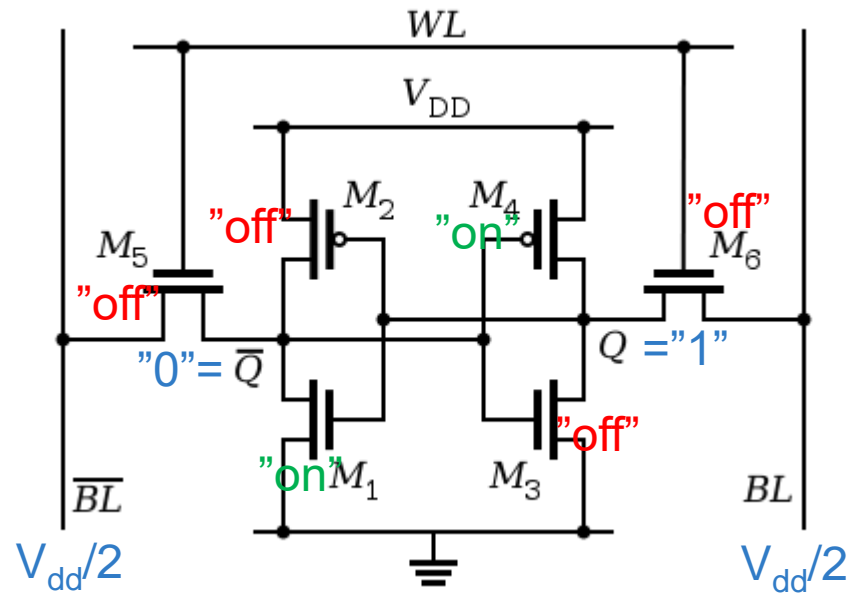

1. Precharge bit lines to  $V_{dd}/2$ 
  - Saves time since lines are long

# SRAM read

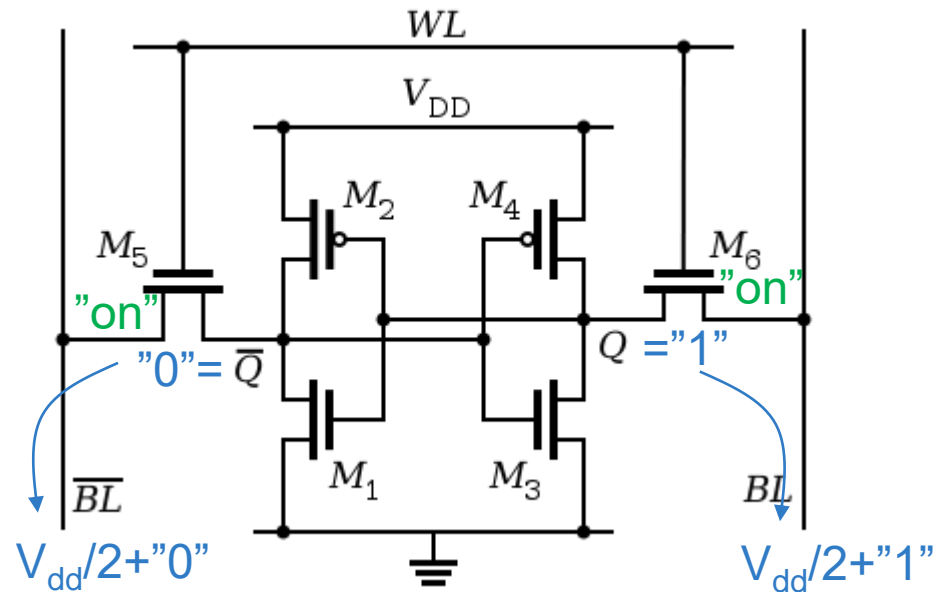

1. Precharge bit lines to  $V_{DD}/2$
2. Turn on  $M_5$ - $M_6$  to take out charge to bit lines
3. Voltage difference between  $BL$  and its conjugate is amplified and sensed. Sign  $\rightarrow$  "0" or "1"
  - If done fast (small voltage change) then the SRAM state recovers (non-destructive read)

# Energy usage and access time

- $E_{cell} = (C_{cell} + 2C_g)V_{dd}^2 \sim 0.3\text{-}2 \text{ fJ/write}$

Gate capacitances,  
Junction capacitances  
Wire capacitances

$C_{cell} \sim 0.5\text{-}1 \text{ fF}$

Gate capacitance of  
access transistors

- **Total energy** dominated by capacitances of metal WL (n) and BL (m) lines

$$E_{write} \approx (n + m)C_{line}V_{dd}^2 \sim 100 \text{ fJ}$$

- **Access time:**

- $t_{SRAM} = (R_{FETon} + R_{line}) * (C_{cell} + C_{line}) \sim 1 \text{ ns}$

# Summary

	DRAM	NAND FLASH	SRAM
Density	$6F^2$	$4F^2$ ( $4/n F^2$ )	$>100F^2$
Speed	10 ns	10 $\mu$ s	1 ns
Storage	Volatile	Non-volatile	Volatile
Energy / write	$10^{-11}$ J	$10^{-9}$ J	$10^{-13}$ J

